

# DIC Design Guide

指導教授：卿文龍


助教：張正宗、陳品崙

# outline


- RTL coding style
  - Blocking and Nonblocking
  - Combinational circuit and Sequential circuit
  - Asynchronous Reset and Synchronous Reset
  - Finite State Machine
  - notes
 
# Blocking and Nonblocking

```
1  module blocking(a, b, c);
2  input  [3:0] a;
3  output [3:0] b, c;
4
5  reg    [3:0] b, c;
6
7  always@(posedge clk)
8  begin
9      b = a;
10     c = b;
11 end
12
13 endmodule
```



 
```
1  module nonblocking(a, b, c);
2  input  [3:0] a;
3  output [3:0] b, c;
4
5  reg    [3:0] b, c;
6
7  always@(posedge clk)
8  begin
9      b <= a;
10     c <= b;
11 end
12
13 endmodule
```



```

1  module blocking(a, b, c);
2  input  [3:0] a;
3  output [3:0] b, c;
4
5  reg    [3:0] b, c;
6
7  always@(posedge clk)
8  begin
9      b = a;
10     c = b;
11 end
12
13 endmodule


```

 

```


1  module nonblocking(a, b, c);
2  input  [3:0] a;
3  output [3:0] b, c;
4
5  reg    [3:0] b, c;
6
7  always@(posedge clk)
8  begin
9      b <= a;
10     c <= b;
11 end
12
13 endmodule

```

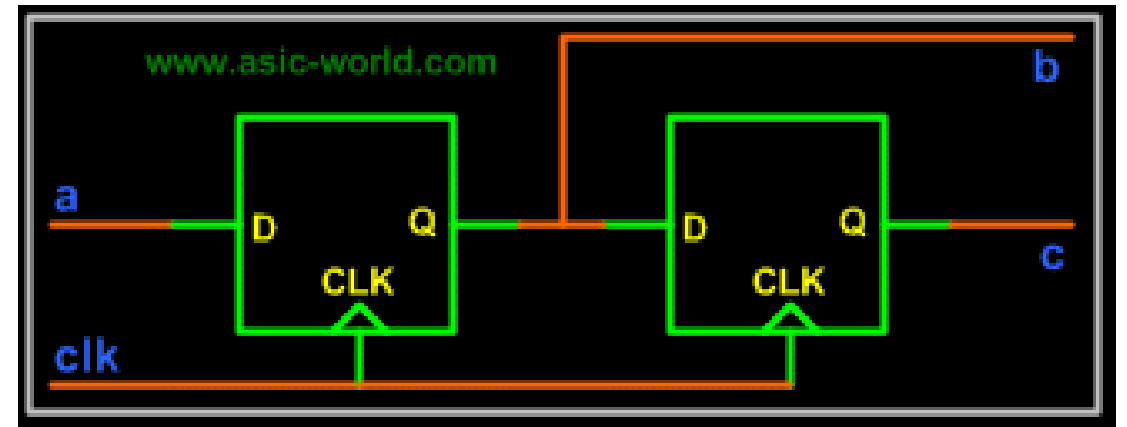
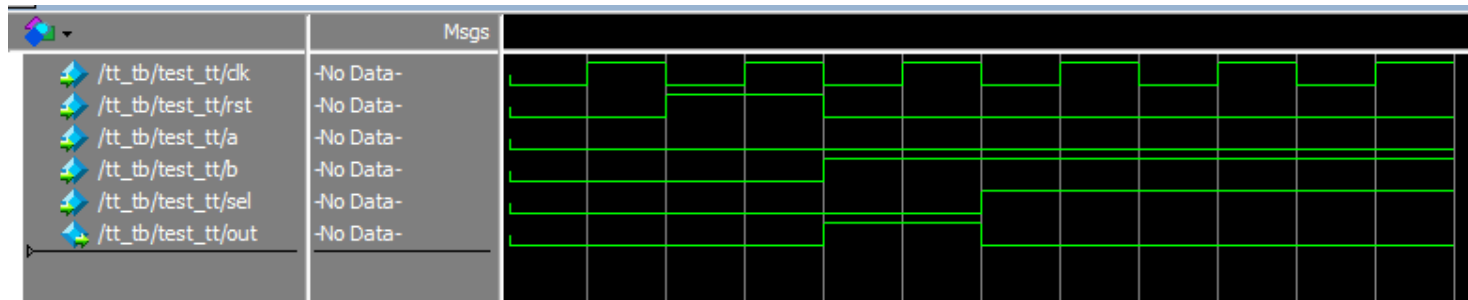
# Combinational circuit and Sequential circuit

- Combinational circuit (組合電路)
  - 輸出訊號會在輸入訊號進來的時候，立即反應(假設gate delay為0)
  - 賦值方式請使用 “=” (blocking)
  - 組合電路可以用assign或是always block去描述，如果是用always block去寫，須宣告成reg，但不為register




```
reg out;  
  
always(*)  
if(sel)  
    out = a;  
else  
    out = b;
```

代表此always block是組合電路(無register)
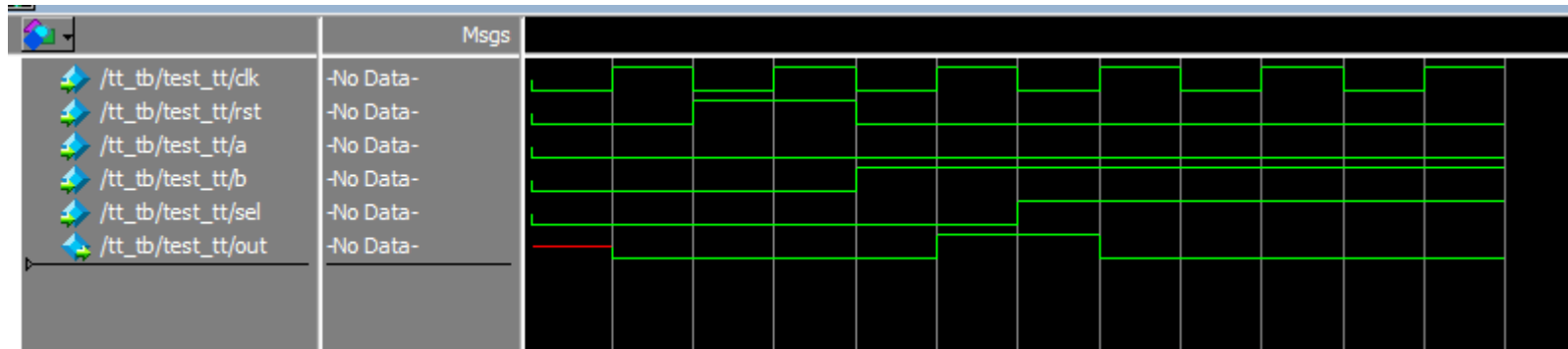
# Combinational circuit and Sequential circuit

- Sequential circuit (時序電路)
  - 輸出訊號會依照輸入訊號先前的狀態在clk正緣輸出
  - 賦值方式請使用”<=”(non-blocking)



```
reg out;  
  
always@(posedge clk)  
if(sel)  
    out <= a;  
else  
    out <= b;
```

代表此always block是時序電路(有register)

# 一個always block 描述一個訊號

- 把訊號分開寫有助於debug，也較容易維護

```
always@(posedge clk or posedge rst)
if(rst)
begin
    counter <= 0;
    so_valid <= 0;
end
else if(cur_st==S0)
    counter <= 0;
else if(cur_st==S1)
    counter <= counter + 1;
else if(counter==4'd7)
    so_valid <= 1;
else
    so_data <= temp[counter];
```



```
always@(posedge clk or posedge rst)
if(rst)
    counter <= 0;
else if(cur_st==S0)
    counter <= 0;
else if(cur_st==S1)
    counter <= counter + 1;
```


```
always@(posedge clk or posedge rst)
if(rst)
    so_valid <= 0;
else if(counter==4'd7)
    so_valid <= 1;
```

```
always@(posedge clk)
    so_data <= temp[counter];
```
 
# 了解自己寫的code會生成什麼電路(架構)


- 組合電路輸出的MUX

```
reg out;  
  
always@(*)  
if(sel)  
    out = a;  
else  
    out = b;
```



- 時序電路輸出的MUX


 
```
reg out;  
  
always@(posedge clk)  
if(sel)  
    out <= a;  
else  
    out <= b;
```





  
# 了解自己寫的code會生成什麼電路(架構)

```
always@(posedge clk or posedge rst)
if(rst)
    counter <= 0;
else
    counter <= counter + 1;
```



 
```
always@(*)
if(rst)
    counter = 0;
else
    counter = counter + 1;
```



 
# 了解自己寫的code會生成什麼電路(架構)

```
always@(*)
if(sel==2'b00)
    out = a;
else if(sel==2'b01)
    out = b;
else if(sel==2'b10)
    out = c;
else
    out = d;
```



 
```
always@(*)
begin
case(sel)
    2'b00 : out = a;
    2'b01 : out = b;
    2'b10 : out = c;
    default : out = d;
endcase
end
```



# Synchronous Reset vs. Asynchronous Reset

 
## ● Synchronous Reset (同步reset)

```
always@(posedge clk)
if(rst)
    counter <= 0;
else
    counter <= counter + 1;
```


 
## ● Asynchronous Reset (非同步reset)


```
always@(posedge clk or posedge rst)
if(rst)
    counter <= 0;
else
    counter <= counter + 1;
```



有reset的話盡量用”非同步reset”

# 控制訊號一定要reset

## ●何謂控制訊號？

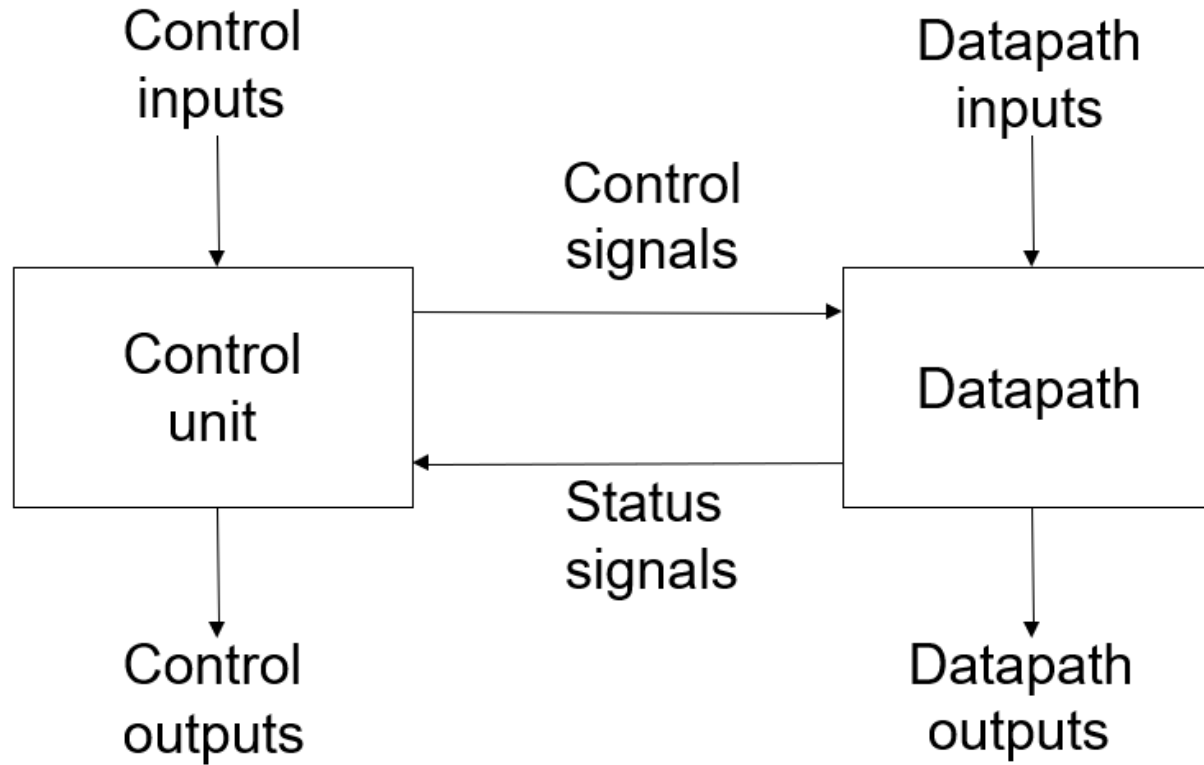

Modern design is composed of  
(1) Datapath and  
(2) Controller (control unit or control path)

# 控制訊號一定要reset

```
always@(posedge clk or posedge rst)
if(rst)
    counter <= 0;
else if(cur_st==S0)
    counter <= 0;
else if(cur_st==S1)
    counter <= counter + 1;
|
```

```
always@(posedge clk or posedge rst)
if(rst)
    so_valid <= 0;
else if(counter==4'd7)
    so_valid <= 1;
```

```
always@(posedge clk)
    so_data <= temp[counter];
```

自己design內新增的訊號，如果該訊號有被拿來做的條件判斷，則視為一種控制訊號。e.g. 狀態機、counter...


輸出給testbench的訊號如果有被拿來作條件判斷也要reset，因為testbench會偵測你design裡的so\_valid是不是1。如果是1，才會去看那時候你的so\_data的值是不是對的。

所以如果一開始so\_valid沒有reset，呈現一個unknown的狀態的話，會誤判你當時的so\_data。

如果還不清楚那些訊號一定要被reset，那就全部訊號都先reset


# Finite State Machine

$$S \rightarrow O$$

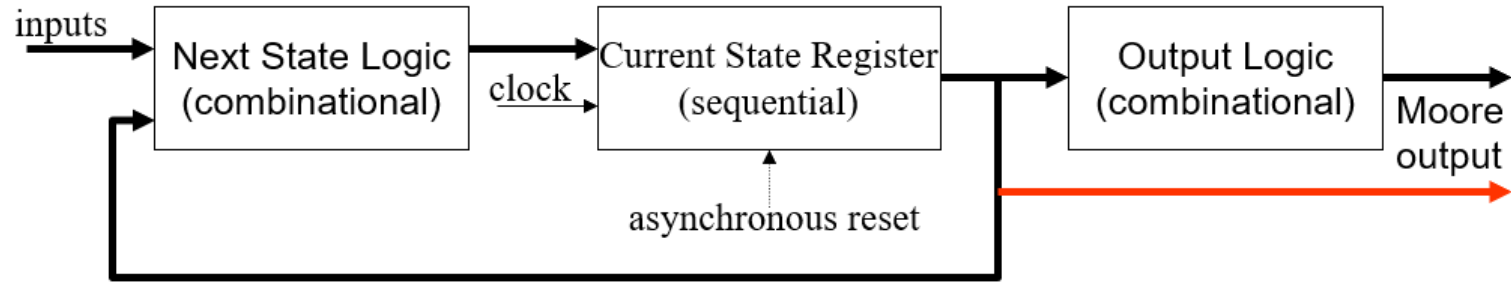

**Moore Machine (state-based machine)**

$$S \times I \rightarrow O$$

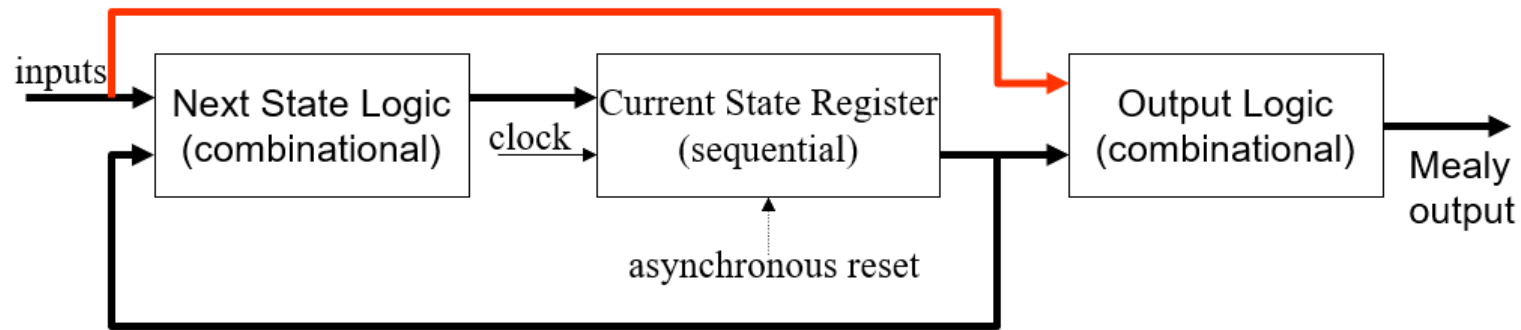

**Mealy Machine (input-based machine)**

# Finite State Machine

```
module FSM(Clock, Reset, Control, Y)
input Clock, Reset, Control;
output [2:0] Y;
```

```
reg [1:0] CurrentState, Nextstate;
reg [2:0] Y;
```

```
parameter ST0 = 2'b00,
          ST1 = 2'b01,
          ST2 = 2'b10,
          ST3 = 2'b11;
```

```
always @(posedge Clock or posedge Reset)
```

```
if (Reset)
```

```
    CurrentState <= ST0;
```

```
else
```

```
    CurrentState <= NextState;
```

Next state  
logic  
(Comb.C.)

State name  
(parameter)

Current State  
Register  
(Seq.C.)

Output  
logic  
(Comb.C.)

```
always @(*)
begin
```

```
    NextState = ST0;
```

```
    case (CurrentState)
```

```
        ST0: NextState = ST1;
```

```
        ST1: if (Control)
```

```
            NextState = ST2;
```

```
        else
```

```
            NextState = ST3;
```

```
        ST2: NextState = ST3;
```

```
        ST3: NextState = ST0;
```

```
    endcase end
```

```
always @(*)
```

```
begin
```

```
    case(CurrentState)
```

```
        ST0: Y = 1;  ST1: Y = 2;
```

```
        ST2: Y = 3;  ST3: Y = 4;
```

```
    endcase
```

```
end endmodule
```

# notes

- 不使用循環次數不確定的迴圈語句，如while等
- 除非是關鍵電路的設計，一般不使用gate level語句來設計，建議採用behavior level語句來設計
- 盡量一個always block 描述一個訊號，會比較不容易出錯
- 對時序電路的描述，應使用non-blocking ( $\leq$ )賦值；對組合電路的描述，應使用 blocking ( $=$ ) 賦值
- 不能在一個以上的always block中對同一個reg賦值，也不能對同一個reg重複使用blocking 與 non-blocking 賦值
- 在組合電路中if-else語句或case語句要把條件寫滿，以免合成出latch
- 避免混合使用 posedge 和 negedge clock觸發