

NCKUES

DIGITAL INTEGRATED CIRCUIT DESIGN

2021 fall

Midterm project

Arithmetic Logic Unit

Professor : Wen-Long Chin


TA : Pin-Wei Chen

VSP LAB

- Design Description

- An arithmetic logic unit (ALU) is a digital circuit that performs arithmetic and logical operations.
- Please design an ALU which performs 8 operations.

- Block Diagram

 

- Specifications

- Top module name : **alu** (File name: alu.v).
- Input ports: **src_a[3:0]**, **src_b[3:0]**, **opcode[2:0]**,
- Output ports: **overflow**, **alu_out[5:0]**, **zero**.

- **Functionality**

- Calculation result (alu_out) please reset to 6'b000000 at the beginning.
- The **zero detection** bit becomes 1 when the calculation result (alu_out) is equal to 6'b000000, otherwise becomes 0.
- The src_a, src_b, alu_out are **signed** number.
- If the calculation result (alu_out) exceed the range that can represent, the **overflow detection** bit will become 1.
- If an overflow occurs, the **maximum or minimum value will be output (saturated output)**.

Ex. $10002 (-8) * 01102 (6) = 10100002 (-48)$

=> overflow = 1, alu_out = 100000 (-32), zero = 0

- Note that when the operation is **left shifting** (<<), overflow detection and saturated output is also needed.
- Note that when the operation is **AND**, the most significant two bits of alu_out (alu_out[5] , alu_out[4]) must be 0.


opcode	ALU operation
000	src_a AND src_b
001	Max (src_a , src_b)
010	LUT (src_a)
011	src_a * src_b
100	src_a + src_b
101	src_a - src_b
110	PERM (src_a , src_b) ,bit permutation
111	src_a << src_b (barrel shift left , $0 \leq \text{src_b} < 8$)

➤ Example

opcode	ALU operation example																																		
000 (AND)	src_a=4'b0001, src_b=4'b1110 → alu_out=6'b000000, zero=1'b1, overflow=1'b0																																		
001 (Max)	src_a=4'b0001, src_b=4'b1110 → alu_out=6'b000001, zero=1'b0, overflow=1'b0																																		
010 (LUT)	<p>Look up table.</p> <table border="1"> <thead> <tr> <th>index</th><th>content</th></tr> </thead> <tbody> <tr><td>0</td><td>31</td></tr> <tr><td>1</td><td>-7</td></tr> <tr><td>2</td><td>0</td></tr> <tr><td>3</td><td>1</td></tr> <tr><td>4</td><td>3</td></tr> <tr><td>5</td><td>10</td></tr> <tr><td>6</td><td>14</td></tr> <tr><td>7</td><td>16</td></tr> <tr><td>8</td><td>-2</td></tr> <tr><td>9</td><td>8</td></tr> <tr><td>10</td><td>21</td></tr> <tr><td>11</td><td>7</td></tr> <tr><td>12</td><td>-17</td></tr> <tr><td>13</td><td>11</td></tr> <tr><td>14</td><td>2</td></tr> <tr><td>15</td><td>8</td></tr> </tbody> </table> <p>alu_out = table[src_a] (此時 src_a 視為無號數) src_a=4'b0010, src_b=4'b1110, → alu_out=6'b000000, zero=1'b1, overflow=1'b0</p>	index	content	0	31	1	-7	2	0	3	1	4	3	5	10	6	14	7	16	8	-2	9	8	10	21	11	7	12	-17	13	11	14	2	15	8
index	content																																		
0	31																																		
1	-7																																		
2	0																																		
3	1																																		
4	3																																		
5	10																																		
6	14																																		
7	16																																		
8	-2																																		
9	8																																		
10	21																																		
11	7																																		
12	-17																																		
13	11																																		
14	2																																		
15	8																																		
011 (*)	src_a=4'b0001, src_b=4'b1110, → alu_out=6'b111111, zero=1'b0, overflow=1'b0 src_a=4'b1000, src_b=4'b0111, → alu_out=6'b100000, zero=1'b0, overflow=1'b1																																		

100(+)	src_a=4'b0001, src_b=4'b1001, → alu_out=6'b111010, zero=1'b0, overflow=1'b0 src_a=4'b0111, src_b=4'b0111, → alu_out=6'b001110, zero=1'b0, overflow=1'b0
101(−)	src_a=4'b0001, src_b=4'b1001, → alu_out=6'b001000, zero=1'b0, overflow=1'b0 src_a=4'b0111, src_b=4'b0011, → alu_out=4'b000100, zero=1'b0, overflow=1'b0
110(PERM)	if src_a is odd, alu_out= {src_a[2],src_b[2],src_a[1],src_b[1],src_a[0],src_b[0]} else {src_b[2],src_a[2],src_b[1],src_a[1],src_b[0],src_a[0]} src_a=4'b0111, src_b=4'b0011, → alu_out=4'b101111, zero=1'b0, overflow=1'b0 src_a =4'b1110, src_b=4'b0001, → alu_out=6'b010101, zero=1'b0, overflow=1'b0
111(<<)	src_a=4'b0111, src_b=4'b0100, → alu_out=6'b011111, zero=1'b0, overflow=1'b1

● waveform

 

testbench 會控制輸入訊號，同學設計的 alu 就是要設法算出對應的輸出然後由 testbench 判斷你輸出的答案是否正確。

➤ 評分標準依以下規定。

1. A 等級為完成測試樣本之所有 RTL simulation 和 Post-synthesis Functional simulation 和 Post-synthesis Timing simulation
 2. B 等級為完成測試樣本之所有 RTL simulation
 3. C 等級為完成測試樣本 50%以上(含)之 RTL simulation
 4. D 等級為完成測試樣本 50%以下之 RTL simulation
- A 等級依照 LUT 個數細分成績，同 LUT 時則依照上傳至 moodle 的時間先後來細分成績
- B 等級依照上傳至 moodle 的時間先後來細分成績
- C、D 等級依照通過測試樣本的比例來細分成績



繳交方式

- 上傳 alu.v 至 moodle，未繳交者以 0 分計。
- 上傳 LUT 個數截圖 (optional)
- 上傳通過 simulation 截圖 (optional)


可將檔案壓縮成.zip 再上傳至 moodle

注意事項

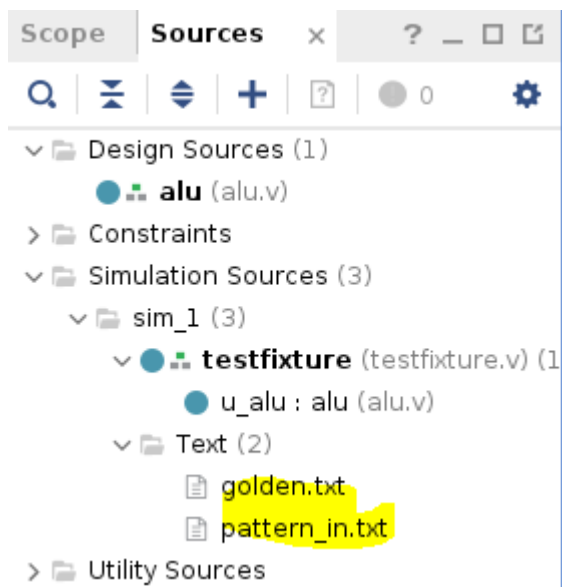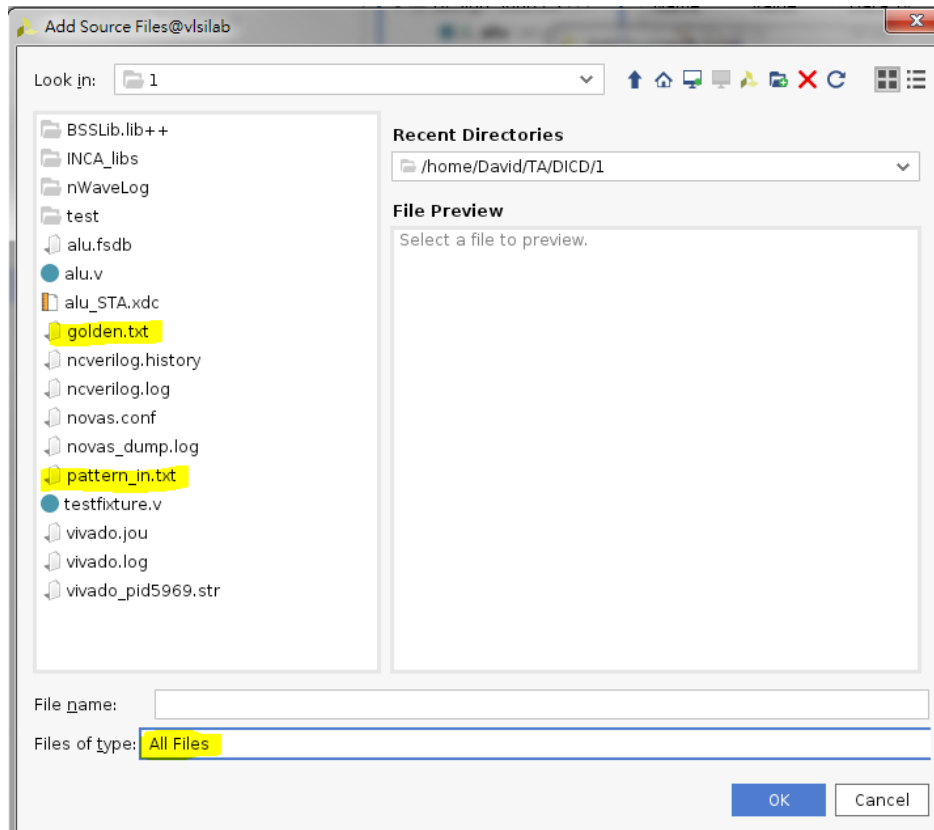1. 請記得將 golden.txt 和 pattern_in.txt 放入 simulation sources



 2. 請勿更改 alu.v 裡面的 input/output 腳位
3. 請注意 simulation 是否確時跑完，若無跑完請按 run all



無論程式(你的 alu.v)功能對錯，要跑到\$finish 才真的有跑完

```

106 ○ $display{"----- ALU check successfully
107 ○ $display{"          $$          "};
108 ○ $display{"          $ $");
109 ○ $display{"          $ $");
110 ○ $display{"          $ $");
111 ○ $display{"          $ $");
112 ○ $display{"$$$$$$$$$ $$$$$$$$");
113 ○ $display{"$$$$$$$ $");
114 ○ $display{"$$$$$$$ $");
115 ○ $display{"$$$$$$$ $");
116 ○ $display{"$$$$$$$ $");
117 ○ $display{"$$$$$$$ $");
118 ○ $display{"$$$$$$$$$$$ $");
119 ○ $display{"$$$$$ $$$$$$$$$$");
120 end
121 ○ else if({err==0}&&{check!=509}) begin
122 ○ $display{"----- Oops! Something wrong with your
123 end
124 ○ else $display{"----- There are %d error
125 ○ $finish ;
126

```

4. 請記得將 xdc 檔放入 constraint sources，要達到 A 等級請務必通過 Post-synthesis Functional simulation 和 Post-synthesis Timing simulation，執行 Post-synthesis simulation 前請先 report timing summary 去確認 setup/hold time 是否 met
(之後會有課堂練習教同學如何跑合成後的 sim)
5. 請勿直接針對特定測資做輸出，會有隱藏測資做驗證
6. 請勿抄襲，若抄襲以 0 分計